

# 计算机组成原理 实验报告

姓名：魏钊 学号：PB18111699 实验日期：2020-5-10

### 一、实验题目：

### 实验三 单周期 CPU

## 二、实验目的:


1. 理解计算机硬件的基本组成、结构和工作原理；
2. 掌握数字系统的设计和调试方法；
3. 熟练掌握数据通路和控制器的设计和描述方法。

### 三、实验平台：

ISE / Vivado (暂不支持其他 Verilog HDL 开发环境的检查)
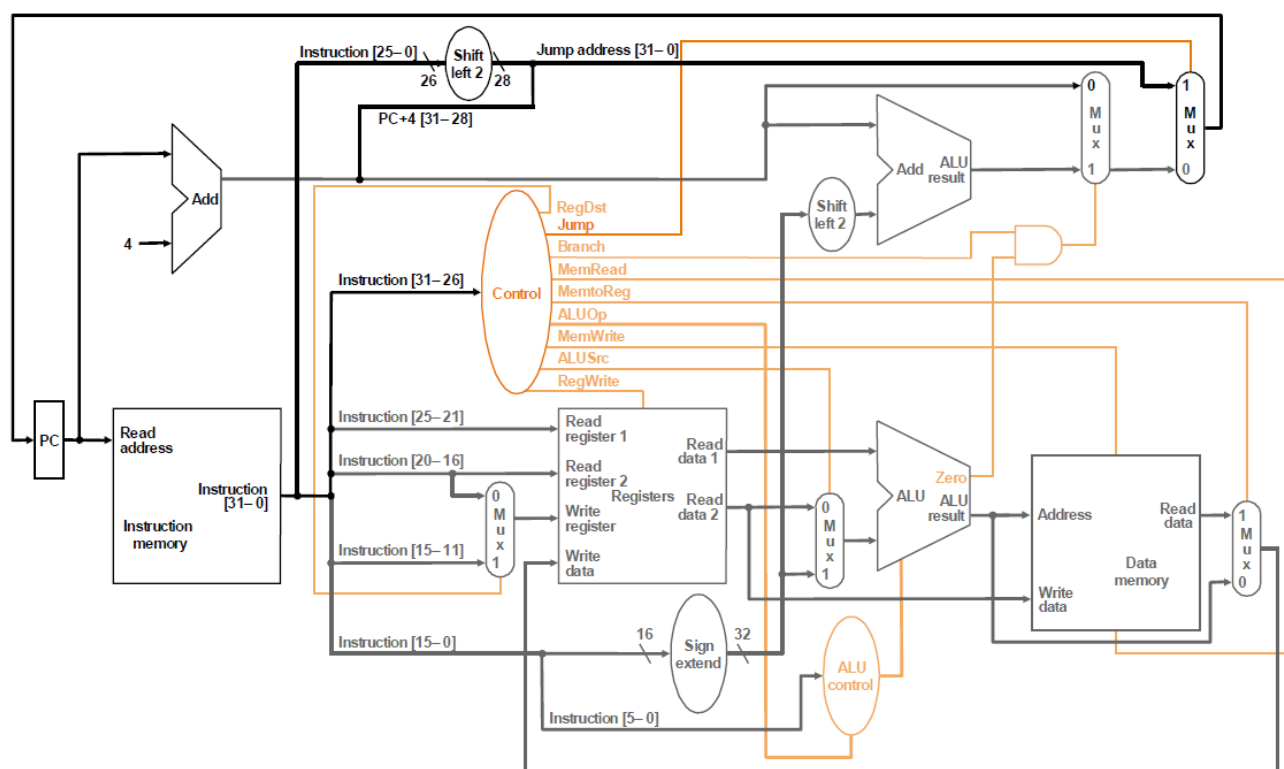
#### 四、实验过程:

首先根据下图设计出 CPU 模块，CPU 中较为重要的是控制器。根据相关指令需要的信号设计控制器。



## CPU:

### Control:

```
23 module Control(  
24     input    [5:0] OpCode,  
25     output    jump,  
26     output    RegDst,  
27     output    Branch,  
28     output    MemRead,  
29     output    MemtoReg,  
30     output    ALUOp,  
31     output    MemWrite,  
32     output    ALUSrc,  
33     output    RegWrite  
34 );  
35 assign RegDst=(OpCode == 6'b0)?1'b1:1'b0;//add时写地址为rd否则为rt  
36 assign jump=(OpCode == 6'b10)?1'b1:1'b0;//是否为J指令  
37 assign Branch=(OpCode == 6'b100)?1'b1:1'b0;//是否为beq指令  
38 assign MemRead=(OpCode == 6'b100011)?1'b1:1'b0;//是否为lw  
39 assign MemtoReg=(OpCode == 6'b100011)?1'b1:1'b0;//是否为lw  
40 assign ALUOp=(OpCode == 6'b100)?1'b1:1'b0;//beq时为减法判断是否为0，否则均为加法  
41 assign MemWrite=(OpCode == 6'b101011)?1'b1:1'b0;//是否为sw  
42 assign ALUSrc=((OpCode == 6'b0)|(OpCode == 6'b100))? 1'b0 : 1'b1;//add和beq时为0，其他为1  
43 assign RegWrite=(OpCode == 6'b1000|OpCode == 6'b0|OpCode == 6'b100011)?1'b1:1'b0;//是否写回寄存器  
44 endmodule
```

### ALUControl:

```
23 module ALUControl(  
24     input    ALUOp,  
25     input    [5:0] Funct,  
26     output[2:0] Sign//ALU控制信号  
27 );  
28 assign Sign=(ALUOp==1'b1) ? 3'b001:3'b000;//ALUOp为1时beq判断两数是否为0，为减法，否则为加法  
29 endmodule
```

### MUX:

```
23 module MUX  
24 #(parameter WIDTH = 32)  
25 (  
26     input    m,  
27     input    [WIDTH-1:0] a,b,  
28     output    [WIDTH-1:0] y  
29 );  
30 assign y=(m==1)?b:a;  
31 endmodule
```

## 寄存器堆:

```
23 module register_file
24     #(parameter WIDTH = 32)
25     (
26         input clk,                //时钟 (上升沿有效)
27         input [4:0] ra0,          //读端口0地址
28         output [WIDTH-1:0] rd0,    //读端口0数据
29         input [4:0] ra1,          //读端口1地址
30         output [WIDTH-1:0] rd1,    //读端口1数据
31         input [4:0] wa,           //写端口地址
32         input we,                 //写使能, 高电平有效
33         input [WIDTH-1:0] wd      //写端口数据
34     );
35     reg [4:0] addr_reg;
36     reg [WIDTH-1:0] mem[0:31];
37
38     assign rd0=mem[ra0]; //异步读
39     assign rd1=mem[ra1];
40
41     always@(*)
42         mem[0]=0;
43
44     always@(posedge clk)
45     begin
46         if(we)
47             if(~(wa==5'b0))
48                 mem[wa]<=wd; //同步写
49         mem[0]=0;
50     end
51 endmodule
```

## ALU:

```
module ALU
    #(parameter WIDTH = 32)
    (
        output reg [WIDTH-1:0] y,    //运算结果
        output reg zf,              //零标志
        output reg cf,              //进位/借位标志
        output reg of,              //溢出标志
        output reg sf,              //最高位是否为1
        input [WIDTH-1:0] a, b,      //两操作数
        input [2:0] m                //操作类型
    );
    always@(*)
    case (m)
        3'b000://加
        begin
            {cf,y}=a+b;
            of=~(a[WIDTH-1]&b[WIDTH-1]&y[WIDTH-1])|(a[WIDTH-1]&b[WIDTH-1]&~y[WIDTH-1]); //溢出标志
            sf=y[WIDTH-1]; //符号标志
            zf=~|y; //零标志
        end
        3'b001://减
        begin
            {cf,y}=a-b;
            of=~(a[WIDTH-1]&b[WIDTH-1]&y[WIDTH-1])|(a[WIDTH-1]&~b[WIDTH-1]&~y[WIDTH-1]); //溢出标志
            sf=y[WIDTH-1]; //符号标志
            zf=~|y; //零标志
        end
    end
```

```

|         3'b010://与
|         begin
|             cf=1'bX;
|             of=1'bX;
|             y=a&b;
|             sf=y[WIDTH-1];//符号标志
|             zf=~|y;//零标志
|         end
|
|         3'b011://或
|         begin
|             cf=1'bX;
|             of=1'bX;
|             y=a|b;
|             sf=y[WIDTH-1];//符号标志
|             zf=~|y;//零标志
|         end
|
|         3'b100://异或
|         begin
|             cf=1'bX;
|             of=1'bX;
|             y=a^b;
|             sf=y[WIDTH-1];//符号标志
|             zf=~|y;//零标志
|         end
|
|         default:
|         begin
|             cf=1'bX;
|             of=1'bX;
|             y=32'bX;
|             sf=1'bX;
|             zf=1'bX;
|         end
|     end
| endcase
| endmodule

```

**指令存储器：256 x 32位ROM，IP例化，分布式存储器**

**数据存储器：256 x 32位RAM，IP例化，分布式存储器**

**CPU:**

为了配合 DBU，输入输出端口做出了改变。

```

module CPU(
    input  rst,
    input  clk,
    input  read, //使用DBU读CPU内部数据使能
    input  [7:0]  m_rf_addr, //地址
    output [31:0] rf_data, //寄存器数据
    output [31:0] m_data, //mem数据
    output reg [31:0] PC,
    output [31:0] PC_next,
    output [31:0] Instruction,
    output [31:0] Read_data1, //寄存器堆读出数据
    output [31:0] Read_data2,
    output [31:0] Alu_out, //ALU输出
    output [31:0] Read_data, //DM中读出数据
    //控制信号
    output jump,
    output RegDst,
    output Branch,
    output MemRead,
    output MemtoReg,
    output [2:0] Sign, //ALU控制
    output MemWrite,
    output ALUSrc,
    output RegWrite,
    output zero
);

```

```

wire [31:0] PC_plus_4;//PC+4
wire [31:0] Jump_addr;//跳转地址
wire [4:0] Write_R;//要写的寄存器地址
wire [31:0] Write_D;//写端口数据
wire [31:0] OP;//ALU的第二个操作数
wire [31:0] add_imm;//指令15-0拓展
wire [31:0] mux0_out;//MUX0的输出
wire zf, cf, of;//ALU相关输出
wire [4:0] rf_addr;
wire [7:0] dm_addr;
reg [31:0] NPC;

//控制信号
wire ALUOp;

assign m_data=Read_data;
assign rf_data=Read_data1;
assign rf_addr=(read==1)?m_rf_addr[4:0]:Instruction[25:21];
assign dm_addr=(read==1)?m_rf_addr:Alu_out[9:2];

IM im(.a(PC[9:2]),.spo(Instruction));
DM dm(.a(dm_addr),.d(Read_data2),.clk(~clk),.we(MemWrite),.spo(Read_data));

Control control(.OpCode(Instruction[31:26]),.jump(jump),.RegDst(RegDst),.Branch(Branch),
    .MemRead(MemRead),.MemtoReg(MemtoReg),.ALUOp(ALUOp),.MemWrite(MemWrite),
    .ALUSrc(ALUSrc),.RegWrite(RegWrite));

ALUControl Alucontrol(.ALUOp(ALUOp),.Funct(Instruction[5:0]),.Sign(Sign));

register_file Registers(.clk(~clk),.ra0(rf_addr),.rd0(Read_data1),.ra1(Instruction[20:16]),
    .rd1(Read_data2),.wa(Write_R),.we(RegWrite),.wd(Write_D));

ALU Alu(.m(Sign),.a(Read_data1),.b(OP),.y(Alu_out),.zf(zf),.cf(cf),.of(of));
//依据数据通路图，从上到下，从左到右MUX
MUX mux0(.m(zero&Branch),.a(PC_plus_4),.b(({add_imm[29:0],2'b00}+PC_plus_4)),.y(mux0_out));
MUX mux1(.m(jump),.a(mux0_out),.b(Jump_addr),.y(PC_next));
MUX mux2(.m(RegDst),.a(Instruction[20:16]),.b(Instruction[15:11]),.y(Write_R));
MUX mux3(.m(ALUSrc),.a(Read_data2),.b(add_imm),.y(OP));
MUX mux4(.m(MemtoReg),.a(Alu_out),.b(Read_data),.y(Write_D));

assign PC_plus_4=PC+32'b100;//PC+4
assign Jump_addr={PC_plus_4[31:28], Instruction[25:0], 2'b00};
assign add_imm={16'b0, Instruction[15:0]};
assign zero=(zf==1'b1&&cf==1'b0&&of==1'b0);

always @(posedge rst or posedge clk)
    if (rst)
        PC <= 32'b0;
    else
        PC <= NPC;

always @(negedge clk or posedge rst)
    if(rst)
        NPC<=32'b0;
    else
        NPC<=PC_next;
endmodule

```

DBU:

按钮去抖动:

```
module Jitter_clr(  
    input clk,  
    input button,  
    output button_clean  
);  
  
parameter jitter_clr_bit=18;  
  
reg [jitter_clr_bit:0] cnt;  
  
always@(posedge clk)  
begin  
    if(button==0)  
        cnt<=0;  
    else  
        if(cnt<(1<<jitter_clr_bit))  
            cnt<=cnt+1;  
    end  
  
    assign button_clean=cnt[jitter_clr_bit];  
endmodule
```

取边沿:

```
module EDG(  
    input clk,  
    input y,  
    input rst,  
    output p  
);  
  
parameter S0=2'b00;  
parameter S1=2'b01;  
parameter S2=2'b10;  
reg [1:0] state=S0,next_state;  
assign p=(state==S1);  
always@(posedge clk or posedge rst)  
begin  
    if(rst)  
        state<=S0;  
    else  
        state<=next_state;  
    end  
    always@(*)  
    begin  
        case(state)  
            S0:if(y)  
                next_state=S1;  
            else  
                next_state=S0;  
            S1:if(y)  
                next_state=S2;  
            else  
                next_state=S0;  
            S2:if(y)  
                next_state=S2;  
            else  
                next_state=S0;  
        endcase  
    end  
endmodule
```

## DBU:

```
module DBU(
    input  succ,
    input  clk,
    input  rst,
    input  read, //读使能
    input  step,
    input  [2:0] sel,
    input  m_rf,
    input  inc,
    input  dec,

    output reg [15:0] led, //16位led
    output [7:0] an, //数码管片选
    output reg [31:0] seg //8个八段数码管
);

wire  step_clean, inc_clean, dec_clean;
wire  step_fin, inc_fin, dec_fin;
wire  clock;
wire  [31:0] PC;
wire  [31:0] PC_next, Instruction, Read_data2, Read_data1, Alu_out;
wire  [31:0] Read_data; //DM中读出数据
reg  [7:0] m_rf_addr;
wire  [31:0] rf_data;
wire  [31:0] m_data;
wire  jump;
wire  RegDst;
wire  Branch;
wire  MemRead;
wire  MementoReg;
wire  [2:0] ALUOp; //ALU控制
wire  MemWrite;
wire  ALUSrc;
wire  RegWrite;
wire  zero;

//相关按钮去抖动
Jitter_clr jitter_clr1(.clk(clk),.button(step),.button_clean(step_clean));
Jitter_clr jitter_clr2(.clk(clk),.button(inc),.button_clean(inc_clean));
Jitter_clr jitter_clr3(.clk(clk),.button(dec),.button_clean(dec_clean));

//相关按钮取边沿
EDG edg1(.clk(clk),.rst(rst),.y(step_clean),.p(step_fin));
EDG edg2(.clk(clk),.rst(rst),.y(inc_clean),.p(inc_fin));
EDG edg3(.clk(clk),.rst(rst),.y(dec_clean),.p(dec_fin));

CPU cpu(.rst(rst),.clk(clock),.Read_data1(Read_data1),.PC(PC),.PC_next(PC_next),
    .Instruction(Instruction),.read(read),.m_rf_addr(m_rf_addr),.rf_data(rf_data),
    .m_data(m_data),.jump(jump),.RegDst(RegDst),.Branch(Branch),.MemRead(MemRead),
    .MementoReg(MementoReg),.Sign(ALUOp),.MemWrite(MemWrite),.ALUSrc(ALUSrc),
    .RegWrite(RegWrite),.zero(zero),.Read_data2(Read_data2),.Alu_out(Alu_out),
    .Read_data(Read_data));

assign clock=(read==1)?1'b0:((succ==1)?clk:step_fin);

always@(posedge clk or posedge rst)
begin
    if(rst)
        m_rf_addr<=8'b0;
    else if((inc_fin==1'b1)&(dec_fin==1'b0))
        m_rf_addr<=m_rf_addr+8'b1;
    else if((dec_fin==1'b1)&(inc_fin==1'b0))
```

```

        m_rf_addr<=m_rf_addr-8'b1;
    else
        m_rf_addr<=m_rf_addr;
    end

always@(*)
begin
    if(sel==3'b0)
    begin
        led={8'b0,m_rf_addr};
        if(m_rf==1)
            seg=m_data;
        else
            seg=rf_data;
        end
    else
    begin
        led={2'b00,sel,m_rf,jump,Branch,RegDst,RegWrite,MemRead,MemtoReg,MemWrite,ALUOp,ALUSrc,zero};
        if(sel==3'b001)
            seg=PC_next;
        else if(sel==3'b010)
            seg=PC;
        else if(sel==3'b011)
            seg=Instruction;
        else if(sel==3'b100)
            seg=Read_data1;
        else if(sel==3'b101)
            seg=Read_data2;
        else if(sel==3'b110)
            seg=Alu_out;
        else if(sel==3'b111)
            seg=Read_data;
        end
    end
end
endmodule

```

## 五、实验结果：

根据提供的 COE 文件，最终在 mem[8]中所存的是 1 即可。

```

module DBU_test;
    reg    succ;
    reg    clk;
    reg    rst;
    reg    read;
    reg    step;
    reg    [2:0] sel;
    reg    m_rf;
    reg    inc;
    reg    dec;
    wire    [15:0] led;
    wire    [7:0] an;//数码管片选
    wire    [31:0] seg;//8个八段数码管
    DBU dbu(.succ(succ),.rst(rst),.clk(clk),.read(read),.step(step),
        .sel(sel),.m_rf(m_rf),.inc(inc),.dec(dec),.led(led),.an(an),.seg(seg));

    always
        #2 clk = ~ clk;
    initial
    begin
        #0 clk=0;
        #0 succ=1'b1;
        #0 step=0;
        #0 rst=1'b1;
        #0 read=1'b0;
        #0 sel=0;
        #0 m_rf=1;
        #0 inc=0;
        #0 dec=0;
        #5 rst=1'b0;
    end
endmodule



```






```

#70 read=1'b1;
#0 inc=1'b1;
#5 inc=1'b0;
#5 inc=1'b1;
#10 $finish;
end
endmodule

```

 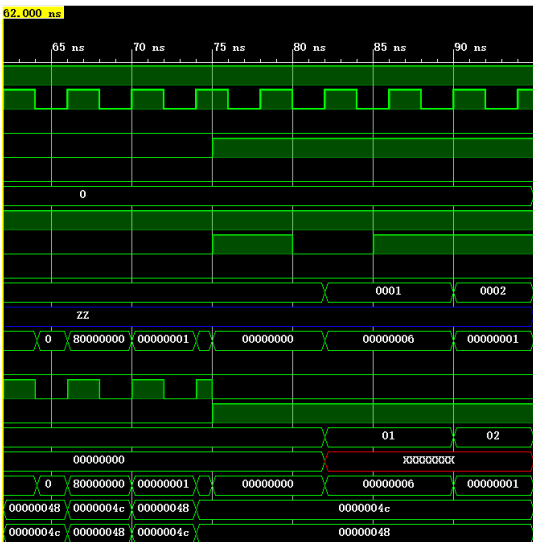

  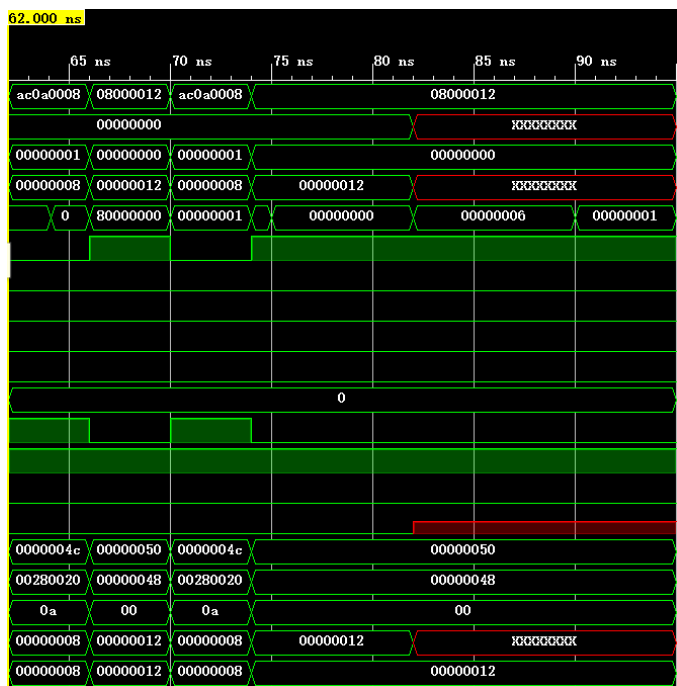

可以看到最终 seg 输出是 1，证明仿真测试成功。

## 六、 心得体会：

通过本次实验理解了计算机硬件的基本组成、结构和工作原理；掌握了数字系统的设计和调试方法；熟练掌握了数据通路和控制器的设计和描述方法。