

计算机组成原理 实验报告

姓名: 魏钊 学号: PB18111699 实验日期: 2020-5-16

一、实验题目:

实验四 多周期 CPU


二、实验目的:

1. 理解计算机硬件的基本组成、结构和工作原理；
2. 掌握数字系统的设计和调试方法；
3. 熟练掌握数据通路和控制器的设计和描述方法。

三、实验平台:

ISE / Vivado (暂不支持其他 Verilog HDL 开发环境的检查)


四、实验过程:

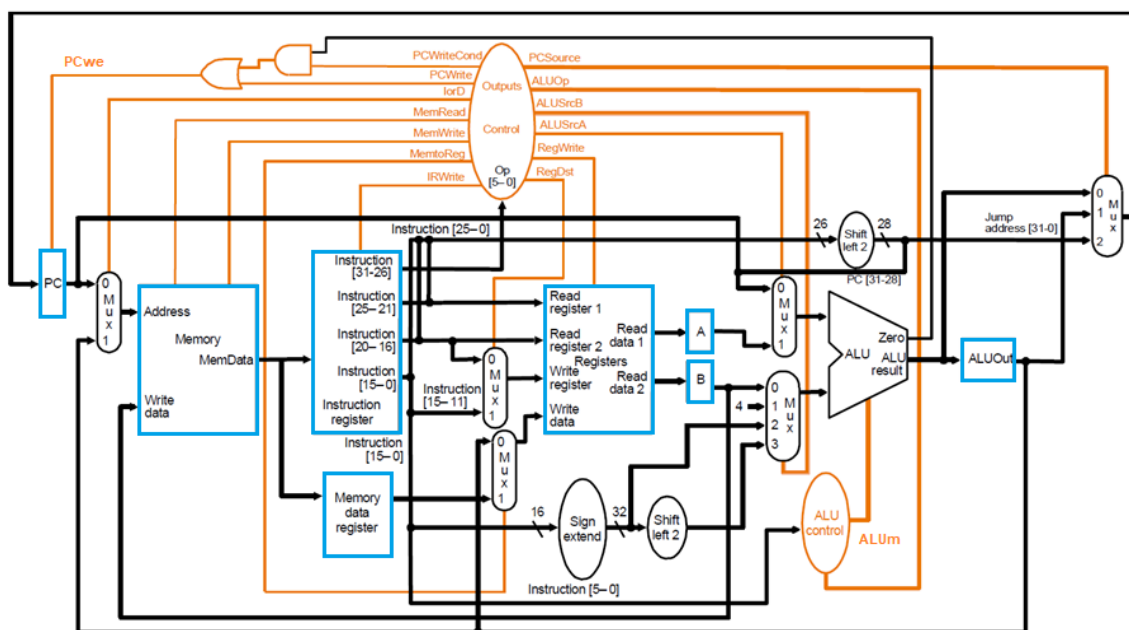

根据上图设计多周期 CPU 相关部件。

控制器:

| Step | R-Type | lw/sw | beq/bne | j |
|------|--|--|--|--|
| IF | $IR = Mem[PC]$ $PC = PC + 4$ | | | |
| ID | $A = Reg[IR[25-21]]$ $B = Reg[IR[20-16]]$ $ALUOut = PC + (SE(IR[15-0]) \ll 2)$ | | | |
| EX | $ALUOut = A \text{ op } B$ | $ALUOut = A + SE(IR[15-0])$ | If $(A == B)$ then $PC = ALUOut$ | $PC = PC[31-28]$ $ $ $(IR[25-0] \ll 2)$ |
| MEM | $Reg[IR[15-11]] = ALUOut$ | $MDR = Mem[ALUOut]$ $Mem[ALUOut] = B$ | | |
| WB | | $Reg[IR[20-16]] = MDR$ | | |

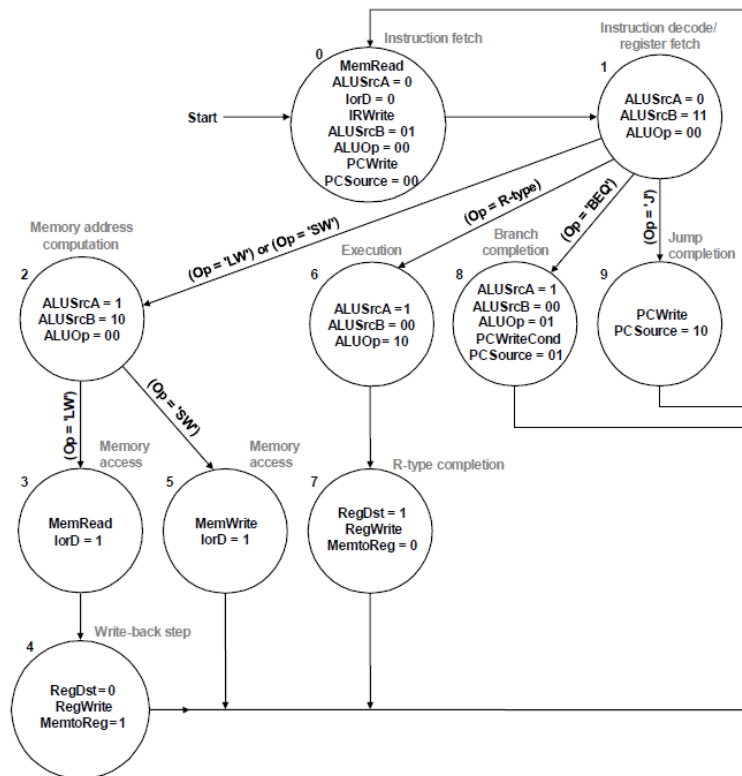

根据状态图及相关信号使能设计控制器：

```

module Control(
    input  clk,
    input  rst,
    input  [5:0]  opcode,
    output reg PCWriteCond,
    output reg PCWrite,
    output reg MemWrite,
    output reg IRWrite,
    output reg RegWrite,
    output reg lorD,
    output reg MemRead,
    output reg MemtoReg,
    output reg [1:0]  PCSource,
    output reg ALUOp,
    output reg [1:0]  ALUSrcB,
    output reg ALUSrcA,
    output reg RegDst
);
    reg [3:0]  state,next_state;

    always@(posedge clk,posedge rst)
    begin
        if(rst)
            state<=4'b0;
        else
            state<=next_state;
    end

    always@(*)

```

```

begin
    case(state)
        4'b0000:
            begin
                MemRead=1'b1;
                lrd=1'b0;
                ALUSrcA=1'b0;
                ALUSrcB=2'b1;
                ALUOp=0;
                PCSource=2'b0;
                PCWrite=1'b1;
                PCWriteCond=1'b0;
                MemWrite=1'b0;
                IRWrite=1'b1;
                RegWrite=1'b0;
                next_state=4'b0001;
            end
        4'b0001:
            begin
                IRWrite=1'b0;
                PCWrite=1'b0;
                ALUSrcA=1'b0;
                ALUSrcB=2'b11;
                ALUOp=0;
                if((opcode==6'b100011) || (opcode==6'b101011)) //lw或sw
                    next_state=4'b0010;
                else if((opcode==6'b000000) || (opcode==6'b001000)) //R指令
                    next_state=4'b0110;
                else if(opcode==6'b000100) //beq
                    next_state=4'b1000;
                else if(opcode==6'b000010) //J
                    next_state=4'b1001;
            end
        4'b0010:
            begin
                ALUSrcA=1'b1;
                ALUSrcB=2'b10;
                ALUOp=0;
                if(opcode==6'b100011)
                    next_state=4'b0011;
                else
                    next_state=4'b0101;
            end
        4'b0011:
            begin
                MemRead=1'b1;
                lrd=1'b1;
                next_state=4'b0100;
            end
        4'b0100:
            begin
                RegDst=1'b0;
                RegWrite=1'b1;
                MemtoReg=1'b1;
                next_state=4'b0000;
            end
        4'b0101:
            begin

```

```

        MemWrite=1'b1;
        lorD=1'b1;
        next_state=4'b0000;
    end
4'b0110:
    begin
        ALUSrcA=1'b1;
        if(opcode==6'b000000)
            ALUSrcB=2'b0;
        else
            ALUSrcB=2'b10;
        ALUOp=0;
        next_state=4'b0111;
    end
4'b0111:
    begin
        if(opcode==6'b000000)
            RegDst=1'b1;
        else
            RegDst=1'b0;
        RegWrite=1'b1;
        MemtoReg=1'b0;
        next_state=4'b0000;
    end
4'b1000:
    begin
        ALUSrcA=1'b1;
        ALUSrcB=2'b0;
        ALUOp=1;

        PCWriteCond=1'b1;
        PCSource=2'b01;
        next_state=4'b0000;
    end
4'b1001:
    begin
        PCWrite=1'b1;
        PCSource=2'b10;
        next_state=4'b0000;
    end
    default:next_state=4'b0000;
endcase
end
endmodule

```

ALUControl:

```

module ALUControl(
    input  ALUOp,
    output[2:0] ALUc//ALU控制信号
);
    assign ALUc=(ALUOp==1'b1) ? 3'b001:3'b000;//ALUOp为1时beq判断两数是否为0，为减法，否则为加法
endmodule

```

ALU:

```
module ALU
#(parameter WIDTH = 32)
(
output reg [WIDTH-1:0] y,      //运算结果
output reg zf,                //零标志
output reg cf,                //进位/借位标志
output reg of,                //溢出标志
output reg sf,                //最高位是否为1
input [WIDTH-1:0] a, b,        //两操作数
input [2:0] m                  //操作类型
);
always@(*)
case (m)
3'b000://加
begin
{cf,y}=a+b;
of=(~a[WIDTH-1]&b[WIDTH-1]&y[WIDTH-1])|(a[WIDTH-1]&b[WIDTH-1]&~y[WIDTH-1]); //溢出标志
sf=y[WIDTH-1]; //符号标志
zf=~|y; //零标志
end

3'b001://减
begin
{cf,y}=a-b;
of=(~a[WIDTH-1]&b[WIDTH-1]&y[WIDTH-1])|(a[WIDTH-1]&b[WIDTH-1]&~y[WIDTH-1]); //溢出标志
sf=y[WIDTH-1]; //符号标志
zf=~|y; //零标志
end

3'b010://与
begin
cf=1'b0;
of=1'b0;
y=a&b;
sf=y[WIDTH-1]; //符号标志
zf=~|y; //零标志
end

3'b011://或
begin
cf=1'b0;
of=1'b0;
y=a|b;
sf=y[WIDTH-1]; //符号标志
zf=~|y; //零标志
end

3'b100://异或
begin
cf=1'b0;
of=1'b0;
y=a^b;
sf=y[WIDTH-1]; //符号标志
zf=~|y; //零标志
end

default:
begin
```

```

        cf=1'b $x$ ;
        of=1'b $x$ ;
        y=32'b $x$ ;
        sf=1'b $x$ ;
        zf=1'b $x$ ;
    end
endcase
endmodule

```

各种 MUX:

```

module MUX_2
#(parameter WIDTH = 32)
(
    input    m,
    input    [WIDTH-1:0] a,b,
    output   [WIDTH-1:0] y
);
assign y=(m==1)?b:a;
endmodule

module MUX_3
#(parameter WIDTH = 32)
(
    input    [1:0]    m,
    input    [WIDTH-1:0] a,b,c,
    output   [WIDTH-1:0] y
);
assign y=(m==2'b0)?a:(m==2'b1)?b:c;
endmodule

module MUX_4
#(parameter WIDTH = 32)
(
    input    [1:0]    m,
    input    [WIDTH-1:0] a,b,c,d,
    output   [WIDTH-1:0] y
);
assign y=(m==2'b0)?a:(m==2'b1)?b:(m==2'b10)?c:d;
endmodule

```

Mem:

指令和数据存储共用一个 RAM 存储器，采用 IP 例化实现，容量为 512 x 32 位的分布式存储器。

寄存器堆:

```
module RF
#(parameter WIDTH = 32)
(
    input clk,                //时钟 (上升沿有效)
    input [4:0] ra0,          //读端口0地址
    output [WIDTH-1:0] rd0,    //读端口0数据
    input [4:0] ra1,          //读端口1地址
    output [WIDTH-1:0] rd1,    //读端口1数据
    input [4:0] wa,            //写端口地址
    input we,                  //写使能, 高电平有效
    input [WIDTH-1:0] wd       //写端口数据
);
    reg [4:0] addr_reg;
    reg [WIDTH-1:0] mem[0:31];

    assign rd0=mem[ra0]; //异步读
    assign rd1=mem[ra1];

    always@(*)
        mem[0]=0;

    always@(posedge clk)
    begin
        if(we)
            if(~(wa==5'b0))
                mem[wa]<=wd; //同步写
        mem[0]=0;
    end
endmodule
```

CPU:

```
module CPU(
    input rst,
    input clk,
    input read,
    input [8:0] m_rf_addr,
    output [1:0] PCSrc,
    output PCwe,
    output lrd,
    output MemWrite,
    output IRWrite,
    output RegDst,
    output MentoReg,
    output RegWrite,
    output [2:0] ALUOp,
    output ALUSrcA,
    output [1:0] ALUSrcB,
    output zero,
    output reg [31:0] Instruction,
    output reg [31:0] Memdata_r,
    output reg [31:0] A,
    output reg [31:0] B,
    output reg [31:0] ALUOut,
    output [31:0] rf_data, //寄存器数据
    output [31:0] m_data //mem数据
);
    reg [31:0] PC;
    wire [31:0] PC_next;
    //reg [31:0] Instruction, Memdata_r; //指令和数据寄存器
    wire [31:0] MemData, ALU_result, Read_data1, Read_data2, Write_data, ALU_OP1, ALU_OP2;
```

```

    wire [4:0] Write_register;
    //reg [31:0] A,B;
    //reg [31:0] ALUOut;
    wire [8:0] Address,addr;
    wire [4:0] rf_addr;
    //控制信号
    //wire PCwe;
    wire PCWriteCond;
    wire PCWrite;
    //wire lorD;
    wire MemRead;
    //wire MemWrite;
    //wire MemtoReg;
    //wire IRWrite;
    //wire [1:0] PCSource;
    wire ALUOp;
    //wire [2:0] ALUm;
    //wire [1:0] ALUSrcB;
    //wire ALUSrcA;
    //wire RegWrite;
    //wire RegDst;
    //wire zero;
    wire zf,cf,of;

    assign addr=(read==1)?m_rf_addr:Address;
    assign m_data=MemData;
    assign rf_data=Read_data1;
    assign rf_addr=(read==1)?m_rf_addr[4:0]:Instruction[25:21];

    Mem mem(.a(addr),.d(B),.clk(clk),.we(MemWrite),.spo(MemData));

    RF Registers(.clk(clk),.ra0(rf_addr),.rd0(Read_data1),
        .ra1(Instruction[20:16]),.rd1(Read_data2),
        .wa(Write_register),.we(RegWrite),.wd(Write_data));

    ALU alu(.y(ALU_result),.zf(zf),.cf(cf),.of(of),.a(ALU_OP1),.b(ALU_OP2),.m(ALUm));

    Control control(.clk(clk),.rst(rst),.opcode(Instruction[31:26]),
        .PCWriteCond(PCWriteCond),.PCWrite(PCWrite),.MemWrite(MemWrite),
        .IRWrite(IRWrite),.RegWrite(RegWrite),.lorD(lorD),.MemRead(MemRead),
        .MemtoReg(MemtoReg),.PCSource(PCSource),.ALUOp(ALUOp),.ALUSrcB(ALUSrcB),
        .ALUSrcA(ALUSrcA),.RegDst(RegDst));

    ALUControl alu_c(.ALUOp(ALUOp),.ALUm(ALUm));

    MUX_2 mux0(.m(lorD),.a(PC[10:2]),.b(ALUOut[10:2]),.y(Address));
    MUX_2 mux1(.m(RegDst),.a(Instruction[20:16]),.b(Instruction[15:11]),.y(Write_register));
    MUX_2 mux2(.m(MemtoReg),.a(ALUOut),.b(Memdata_r),.y(Write_data));
    MUX_2 mux3(.m(ALUSrcA),.a(PC),.b(A),.y(ALU_OP1));
    MUX_4 mux4(.m(ALUSrcB),.a(B),.b(32'b100),.c({16'b0,Instruction[15:0]}),.d({14'b0,Instruction[15:0],2'b0}),.y(ALU_OP2));
    MUX_3 mux5(.m(PCSource),.a(ALU_result),.b(ALUOut),.c({PC[31:28],Instruction[25:0],2'b00}),.y(PC_next));

    assign PCwe=((PCWrite==1)||((PCWriteCond==1)&&(zero==1)));
    assign zero=(zf==1&&cf==0&&of==0);

    always@(posedge clk,posedge rst)
    begin
        Memdata_r<=MemData;

```



```

        ALUOut<=ALU_result;
        A<=Read_data1;
        B<=Read_data2;
    }
    if(rst)
        PC<=32'b0;
    else
        if(PCwe)
            PC<=PC_next;
        if(IRWrite)
            Instruction<=MemData;
    end
endmodule

```

DBU:

```

module DBU(
    input  succ,
    input  clk,
    input  rst,
    input  read, //读使能
    input  step,
    input  [2:0] sel,
    input  m_rf,
    input  inc,
    input  dec,
    output [15:0] led, //16位led
    output [7:0] an, //数码管片选
    output reg [31:0] seg //8个八段数码管
);

wire  step_clean, inc_clean, dec_clean;
wire  step_fin, inc_fin, dec_fin;
wire  clock;
wire  [31:0] PC;
reg  [8:0]  m_rf_addr;
wire  [31:0] rf_data;
wire  [31:0] m_data;
wire  [31:0] Instruction, Memdata_r, A, B, ALUOut;

wire  [1:0]  PCSource;
wire  PCwe;
wire  lorD;
wire  MemWrite;
wire  IRWrite;
wire  RegDst;

wire  MentoReg;
wire  RegWrite;
wire  [2:0]  ALUu;
wire  ALUSrcA;
wire  [1:0]  ALUSrcB;
wire  zero;
//相关按钮去抖动
Jitter_clr jitter_clr1(.clk(clk),.button(step),.button_clean(step_clean));
Jitter_clr jitter_clr2(.clk(clk),.button(inc),.button_clean(inc_clean));
Jitter_clr jitter_clr3(.clk(clk),.button(dec),.button_clean(dec_clean));
//相关按钮取边沿
EDG edg1(.clk(clk),.rst(rst),.y(step_clean),.p(step_fin));
EDG edg2(.clk(clk),.rst(rst),.y(inc),.p(inc_fin));
EDG edg3(.clk(clk),.rst(rst),.y(dec_clean),.p(dec_fin));

CPU cpu(rst, clock, read, m_rf_addr, PCSource, PCwe, lorD, MemWrite, IRWrite, RegDst,
        MentoReg, RegWrite, ALUu, ALUSrcA, ALUSrcB, zero, Instruction, Memdata_r, A, B,
        ALUOut, rf_data, m_data);
assign clock=(read==1)?1'b0:((succ==1)?clk:step_fin);
assign led=(sel==0)?{7'b0, m_rf_addr}:{PCSource, PCwe, lorD, MemWrite, IRWrite, RegDst, MentoReg, RegWrite, ALUu, ALUSrcA, ALUSrcB, zero};

always@(posedge clk or posedge rst)
begin
    if(rst)
        m_rf_addr<=9'b0;
    else if((inc_fin==1'b1)&(dec_fin==1'b0))
        m_rf_addr<=m_rf_addr+9'b1;
    else if((dec_fin==1'b1)&(inc_fin==1'b0))
        m_rf_addr<=m_rf_addr-9'b1;
end


```


```





        else
            m_rf_addr<=m_rf_addr;
end
always@(*)
begin
    if(sel==3'b0)
        begin
            if(m_rf==1)
                seg=m_data;
            else
                seg=rf_data;
        end
    else
        begin
            if(sel==3'b001)
                seg=PC;
            else if(sel==3'b010)
                seg=Instruction;
            else if(sel==3'b011)
                seg=Memdata_r;
            else if(sel==3'b100)
                seg=A;
            else if(sel==3'b101)
                seg=B;
            else if(sel==3'b110)
                seg=ALUOut;
            else if(sel==3'b111)
                seg=0;
        end
    end
end
endmodule


```

五、实验结果：

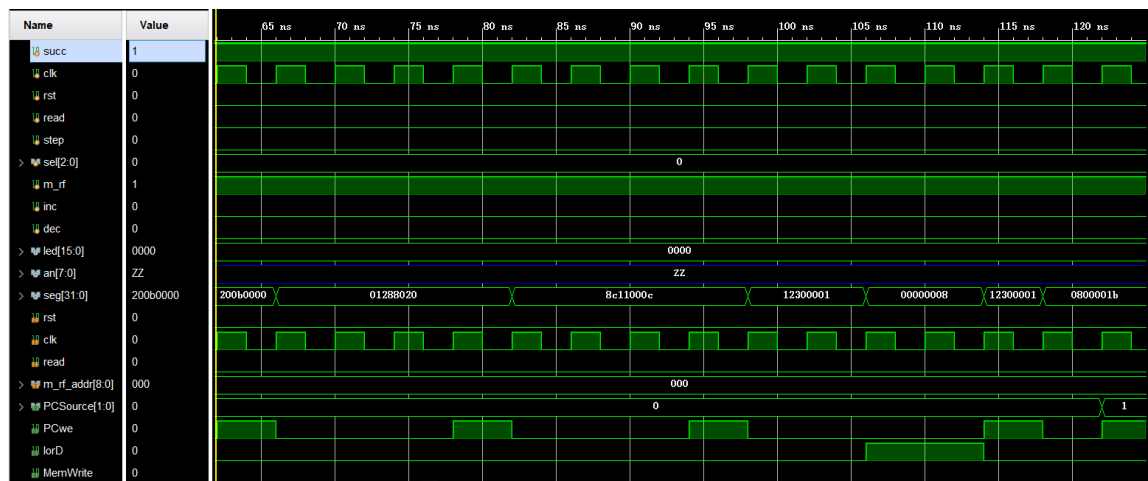

 

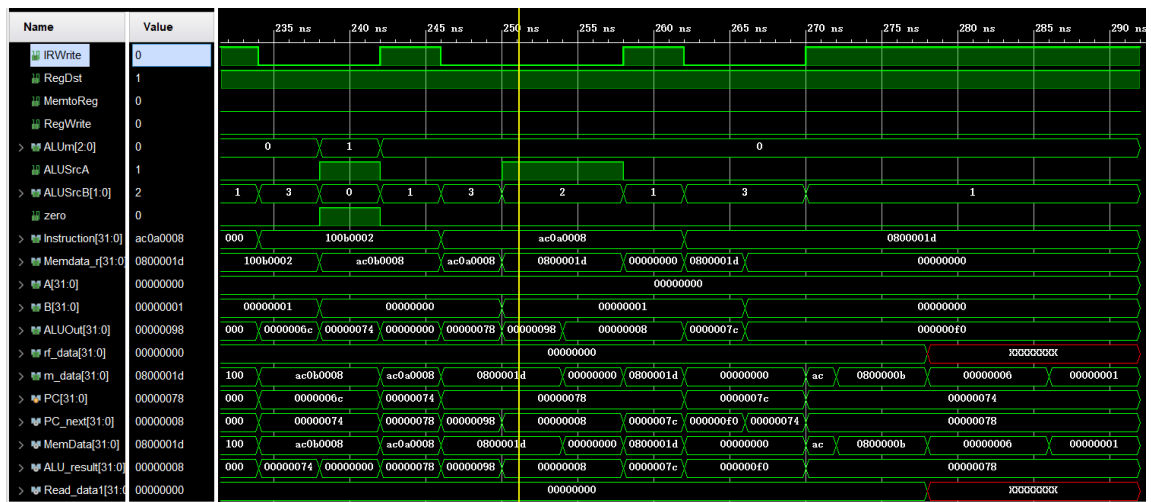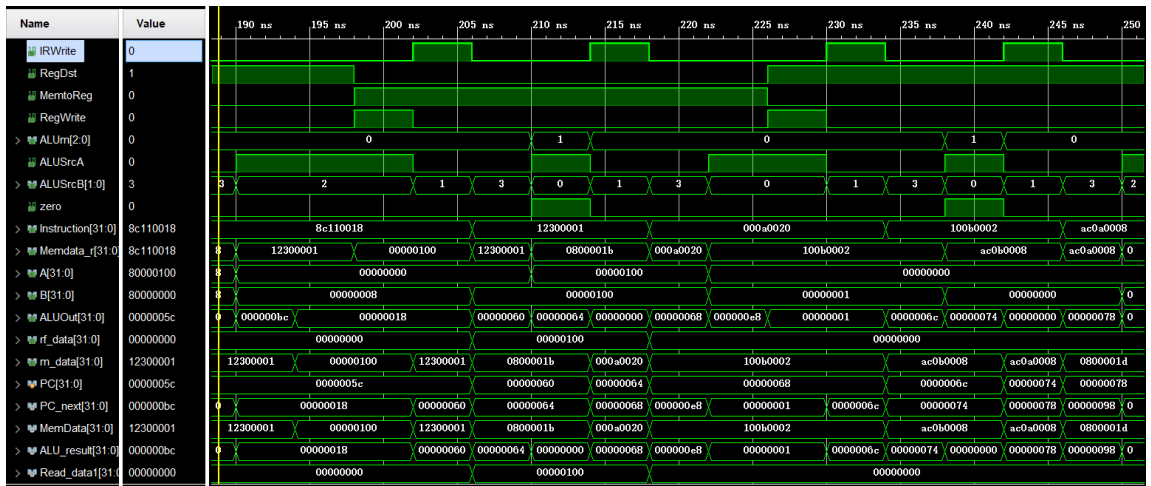 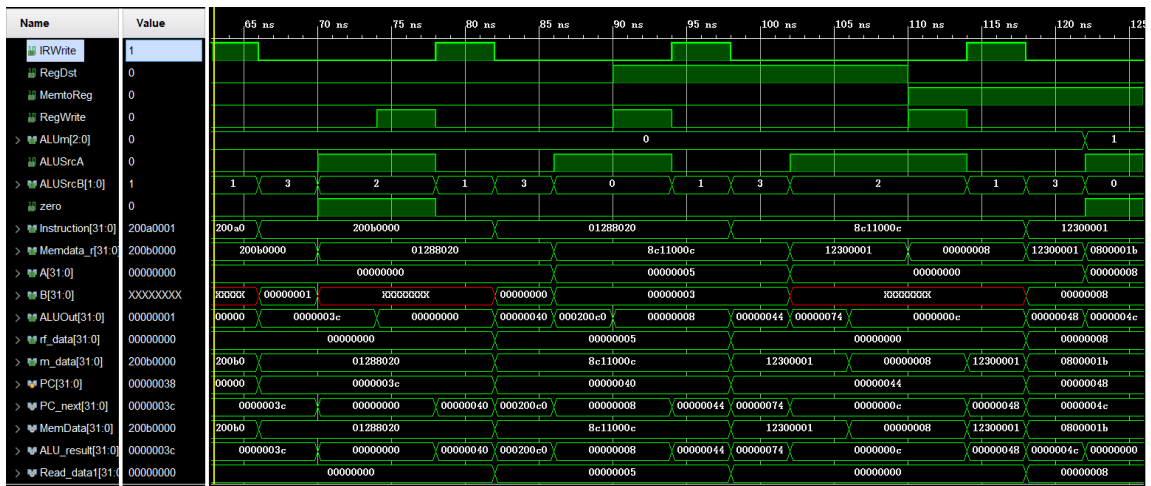

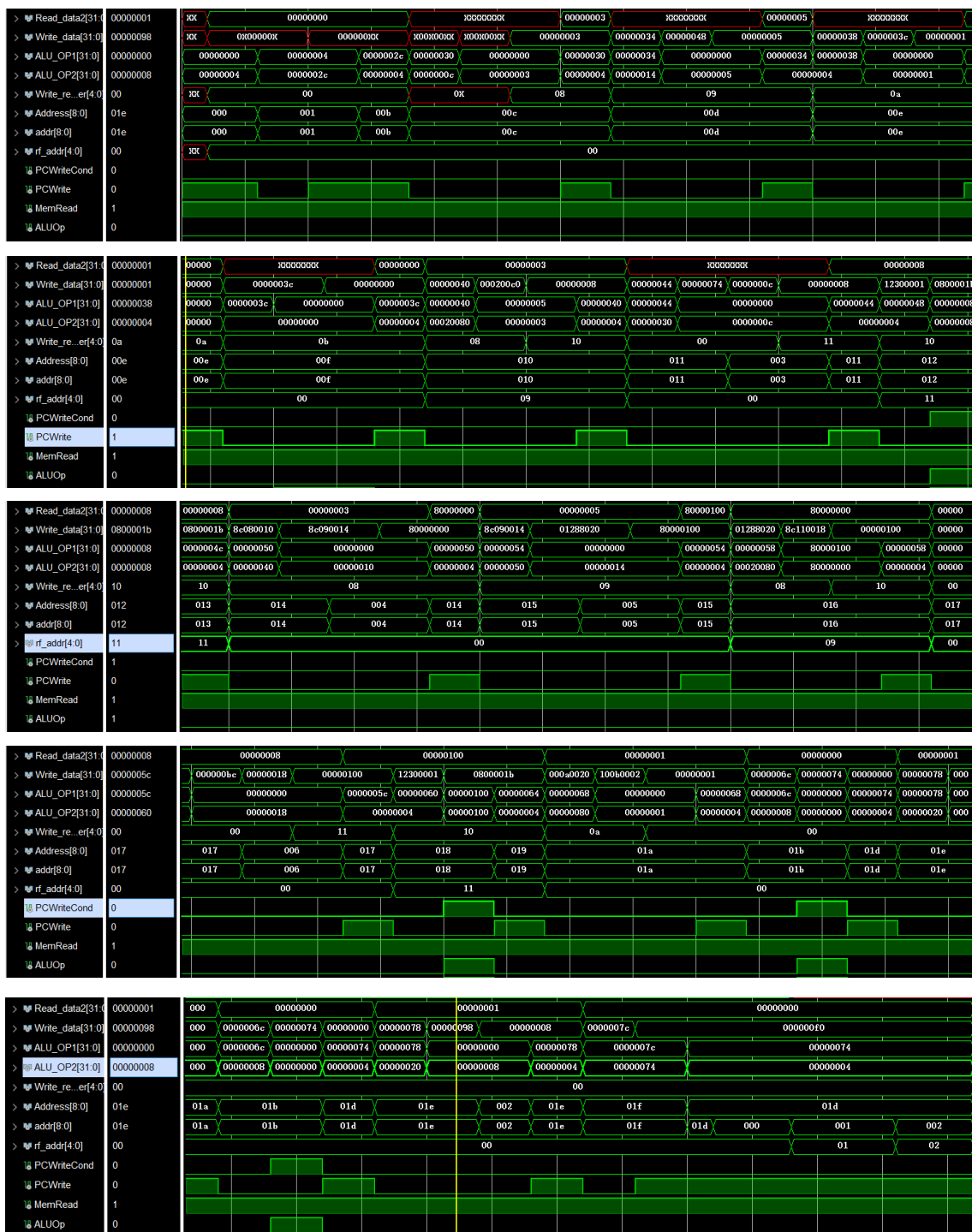

六、心得体会：

通过本次实验理解了计算机硬件的基本组成、结构和工作原理；掌握了数字系统的设计和调试方法；熟练掌握了数据通路和控制器的设计和描述方法。